

Finite State Machines

CS 64: Computer Organization and Design Logic
Lecture #16

Ziad Matni
Dept. of Computer Science, UCSB

Administrative

- *LESS THAN 2 weeks left!!!!!!*
OMGOMGOMGOMGOMGOMG!!!!!!
- Final exam is on Wednesday, June 13th from 12:00 – 3:00 PM.
 - Details will be given next week

Lecture Outline

- Finite State Machines
 - Moore vs. Mealy types
 - State Diagrams
 - “One Hot” Method

Any Questions From Last Lecture?

If a combinational logic circuit is an implementation of a ***Boolean function***,


then a sequential logic circuit can be considered an implementation of a ***finite state machine***.

Finite State Machines (FSM)

- An **abstract machine** that can be in **exactly one of a finite number of states at any given time**
- It's a very simple model of a computational machine, unlike Pushdown Automata and Turing Machines
 - You'll discover these in other CS upper-div classes


Finite State Machines (FSM)

 - The FSM can change from one state to another in **response to some external inputs**
- The change from one state to another is called a **transition**.



- An FSM is defined by a list of its states, its initial state, and the conditions for each transition.


Example of a Simple FSM: The Turnstile

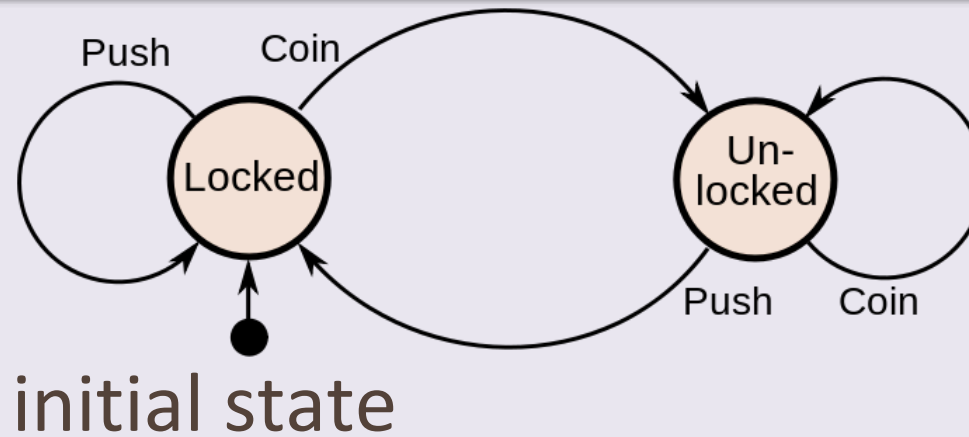

State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.


Example of a Simple FSM: The Turnstile

 


State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.
Locked	Push	Locked	Nothing – you’re locked! 😊
Unlocked	Coin	Unlocked	Nothing – you just wasted a coin! 😊
Unlocked	Push	Locked	When the customer has pushed through, locks the turnstile.

General Form of FSMs

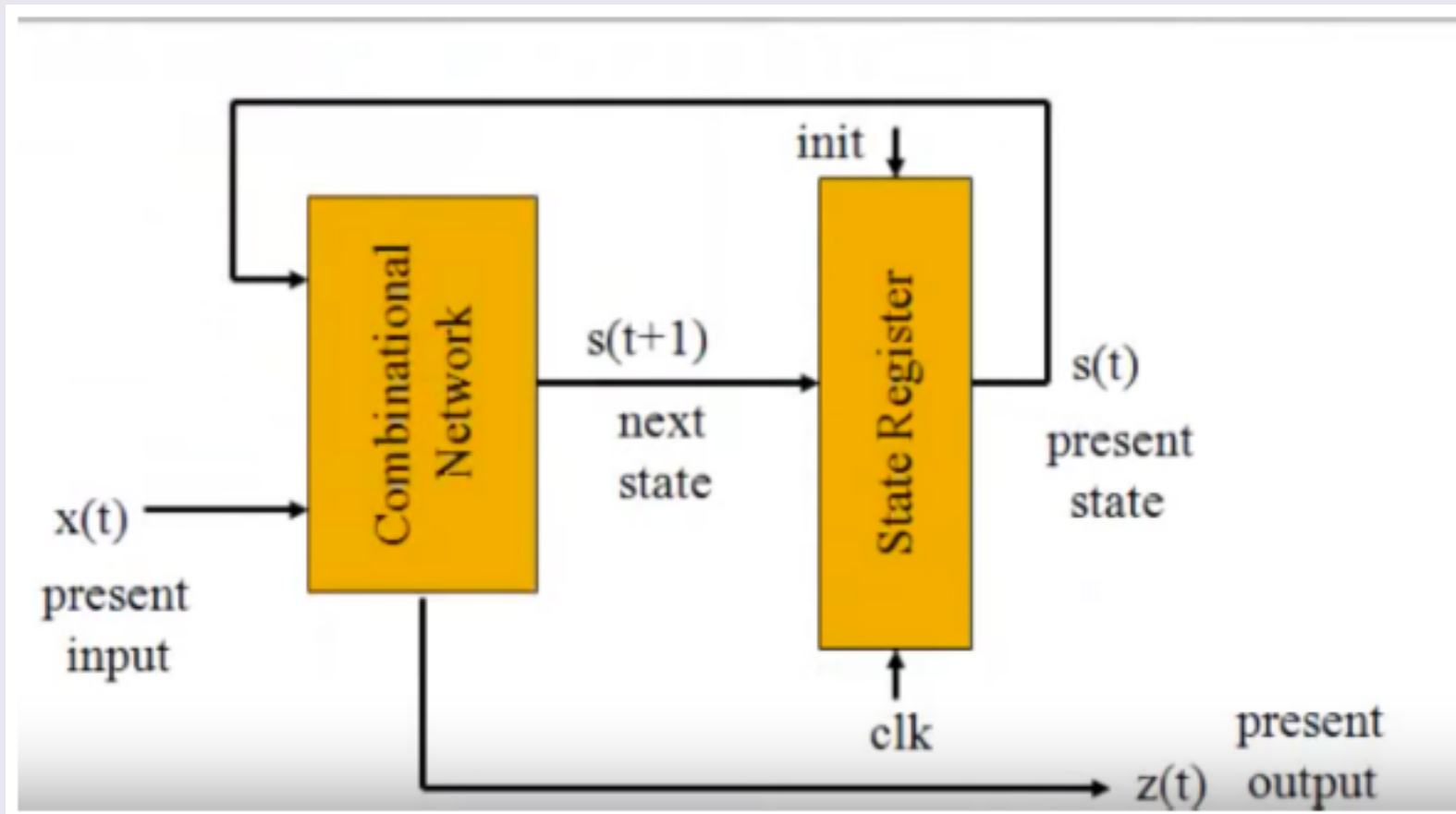

Example

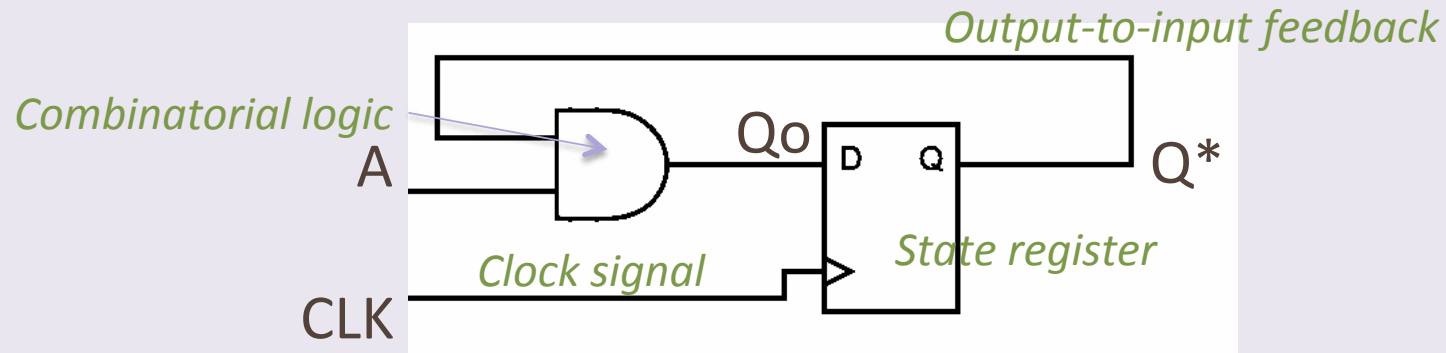

$$Q^* = Q_0 \cdot A$$

On the next rising edge of the clock, the output of the D-FF Q (Q^*) will become the previous value of Q (Q_0) **AND** the value of input A


FSM Types

There are 2 types/models of FSMs:

- **Moore machine**
 - Output is function of present state only
- **Mealy machine**
 - Output is function of present state *and* present input


Moore Machine

Output is function of present state only

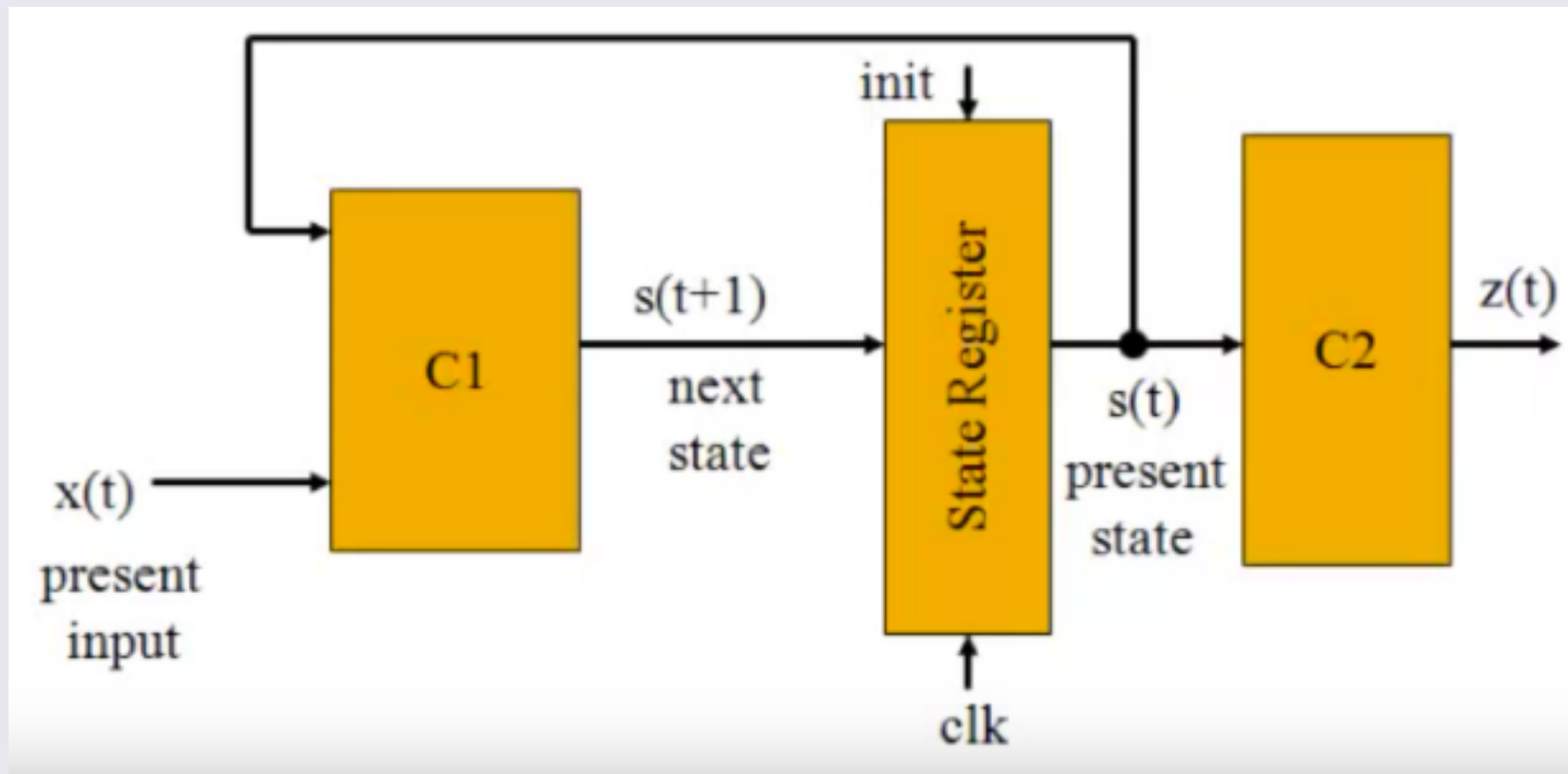

Example of a Moore Machine (with 1 state)

Output is function of present state only

 


$$Z = \overline{(Q^* + B)} = \overline{(Q_0 \cdot A + B)}$$

On the next rising edge of the clock, the output of the entire circuit (Z) will become

(the previous value of Q (Q_0) **AND** the value of input A)
NOR B


Mealy Machine

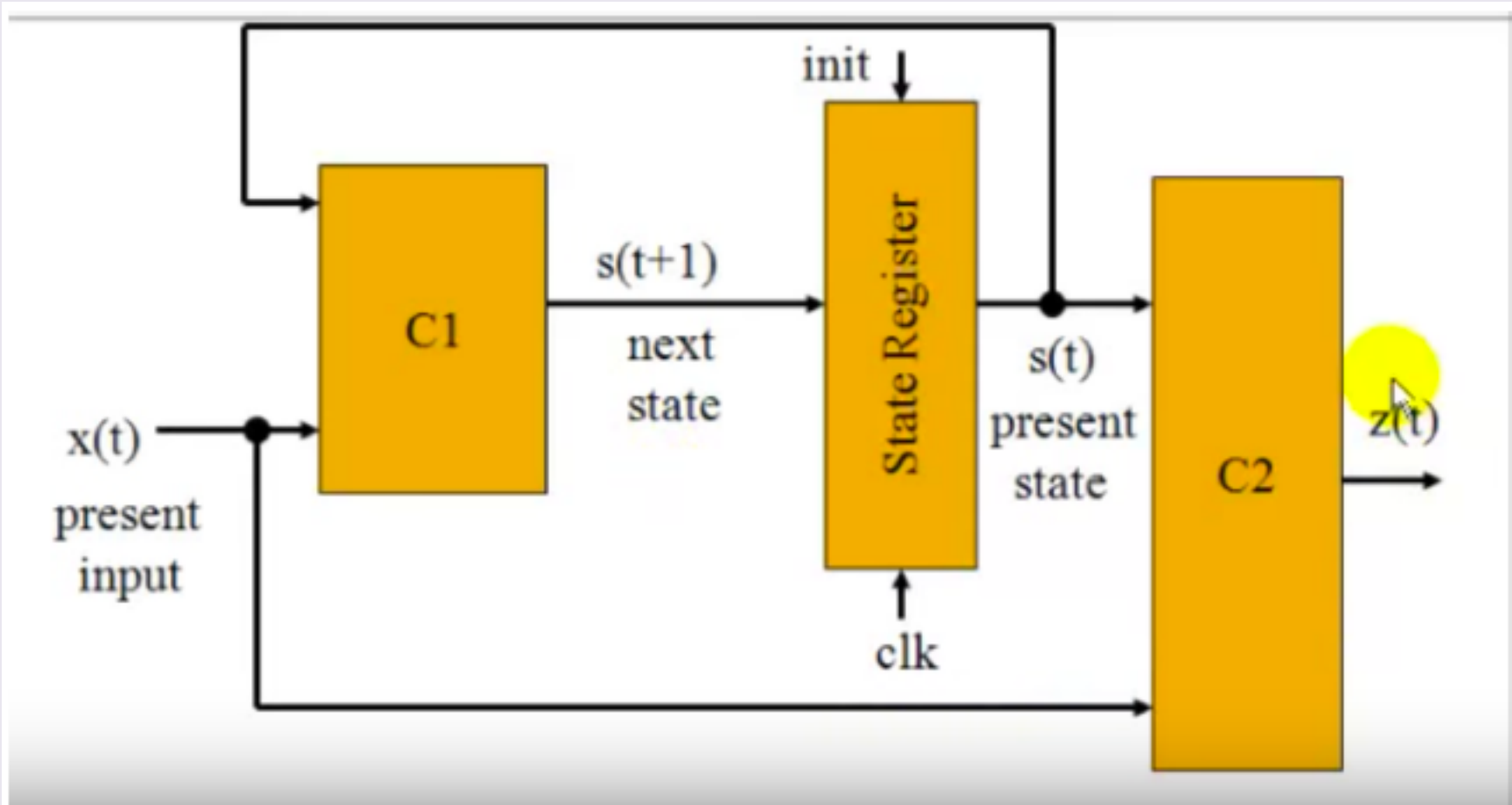Output is function of present state and present input



 Example of a Mealy Machine (with 1 state)

Output is function of present state and present input




$$Z = (Q^* + A + B) = (Q_0 \text{ XOR } A) + (A + B)$$

On the next rising edge of the clock, the output of the entire circuit (Z) will become ...etc...

Diagramming State Machines

 - A simple FSM example
- 2 states:
 - Door opened
 - Door closed
- This is called a **state diagram**



Example of a Moore Machine 1

WASHER_DRYER

- Let's "build" a sequential logic FSM that acts as a controller to a *simplistic* washer/dryer machine
- This machine takes in various inputs in its operation (we'll only focus on the following sensor-based ones):

Coin put in (vs it isn't)

Timer is under 30 minutes (vs it isn't)

Soap is present (vs used up)

Wetness indicator (vs clothes are dry)

- This machine also issues outputs while running:

"Timer Begin" indicator

"Fill-Water" indicator

"Drain-Then-Refill" indicator

"Drain Completely" indicator

Example of a Moore Machine 1

WASHER_DRYER

- Before we begin, the machine is in an initial state that is waiting for you to insert a coin. We'll call that the "Initial State"
- The machine will start a washer timer as soon as a coin is inserted.
 - By issuing an output, "Timer Begin"
- The timer is controlled by a signal (i.e. input var) called **TIMER_LT_30**, which is always initialized to be 1 (i.e. True).
- We thus transition from "Initial State" to "Wash State"

Example of a Moore Machine 1

WASHER_DRYER

- Wash State: This will output a signal to fill the washer with water (**FILL_WATER**).
- As long as the timer is below 30 mins (**TIMER_LT_30 = 1**), the cycle continues.
- When the timer surpasses 30 mins (i.e. **TIMER_LT_30 = 0**), this state will end
- We thus transition from “Wash State” to “Rinse State”

Example of a Moore Machine 1

WASHER_DRYER



- Rinse State: This will output a signal to drain the water and then refill with new water (**DRAIN_REFILL = 1**).
- As long as the soap sensor is on (**SOAP = 1**), the cycle continues.
- When the soap sensor turns off (i.e. **SOAP = 0**), this state will end
- We thus transition from “Rinse State” to “Dry State”

Example of a Moore Machine 1

WASHER_DRYER


- Dry State: This will output a signal to drain the water for good and begin drying (**DRAIN = 1**).
- As long as the wet clothes sensor is on (**WET = 1**), the cycle continues.
- When the wet clothes sensor is off (**WET = 0**), we will stop!
- This means going back to the “**Initial State**”

State Diagram for Washer-Dryer Machine

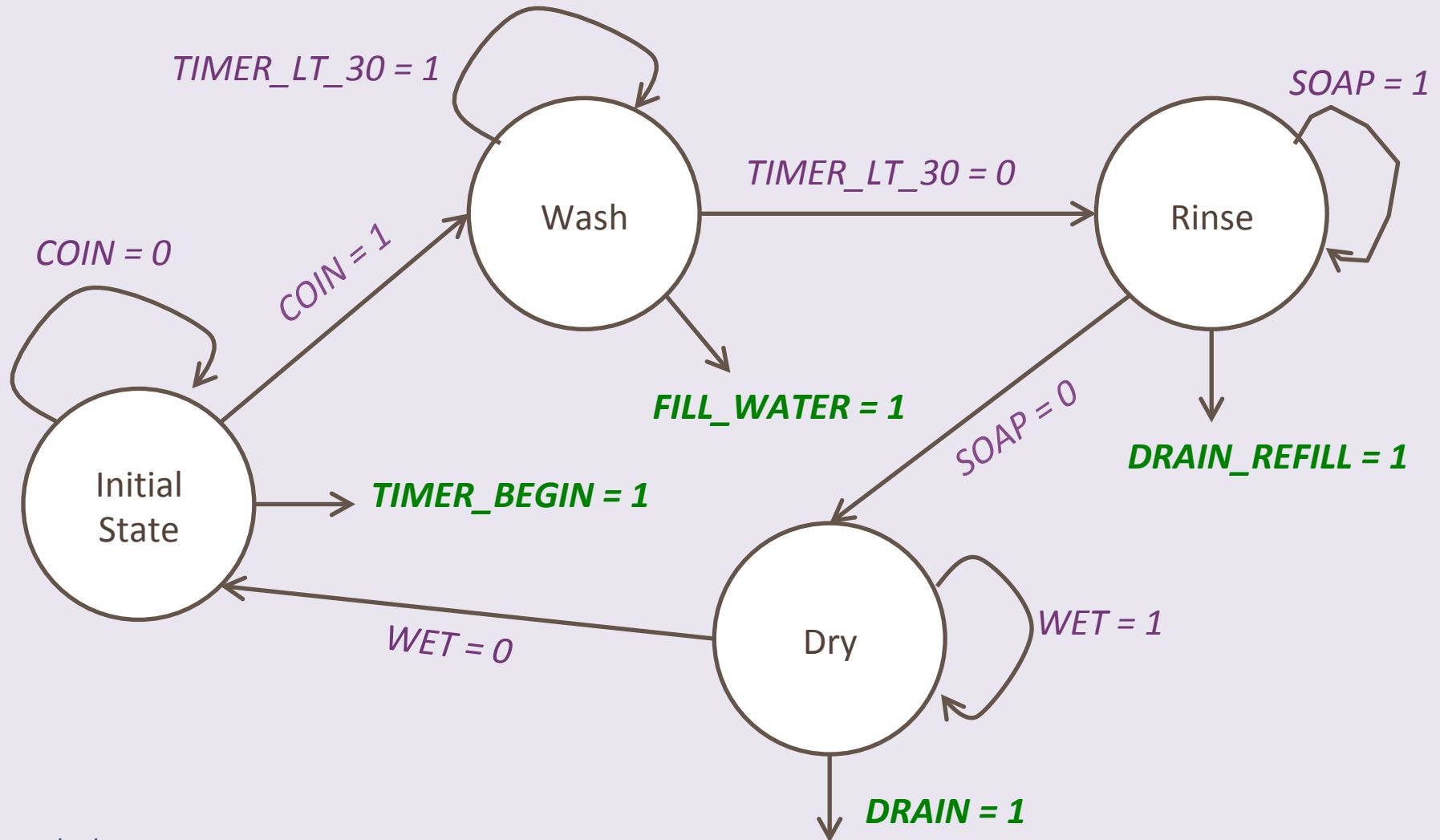 

Unconditional Transitions

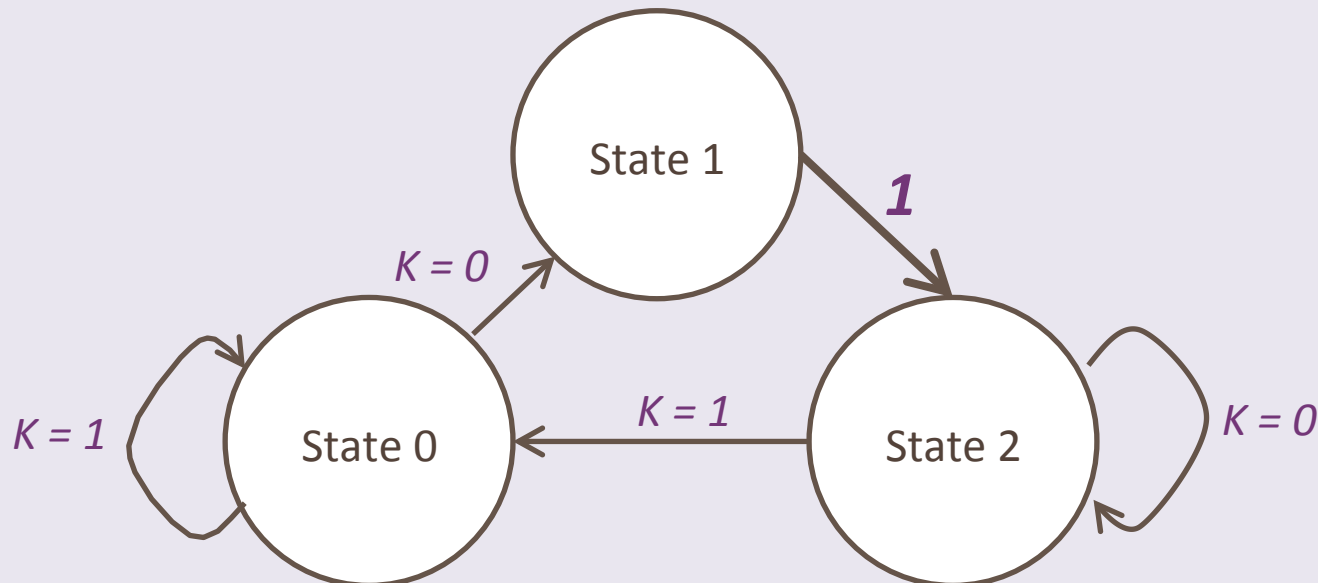- Sometimes the transition is unconditional
 - Does not depend on any input – it just happens
- We then diagram this as a “1” (for “always does this”)



Representing The States

- How many bits do I need to represent all the states in this Washer-Dryer Machine?

- There are 4 unique states (including “init”)
 - So, 2 bits

- If my state machine will be built using a memory circuit (most likely, a D-FF), how many of these should I have?

- 2 bits = 2 D-FFs

- There is another scheme to do this called “One Hot Method”.
 - More on this later...


State	S1	S0
Initial	0	0
Wash	0	1
Rinse	1	0
Dry	1	1

Example of a Moore Machine 2

DETECT_1101

- Let's build a sequential logic FSM that always detects a specific serial sequence of bits: **1101**
- We'll start at an "Initial" state (S0)
- We'll first look for a **1**. We'll call that "State 1" (S1)
 - Don't go to S1 if all we find is a **0**!
- We'll then keep looking for another **1**. We'll call that "State 11" (S2)
- Then... a **0**. We'll call that "State 110" (S3)
- Then another **1**.
We'll call that "State 1101"(S4) – this will output a **FOUND** signal
- We will always be detecting "1101" (it doesn't end)
- Example: if the input stream is **111101110101101000011111011011**
we detect "1101" at ↑ ↑ ↑ ↑ ↑

State Diagram 2

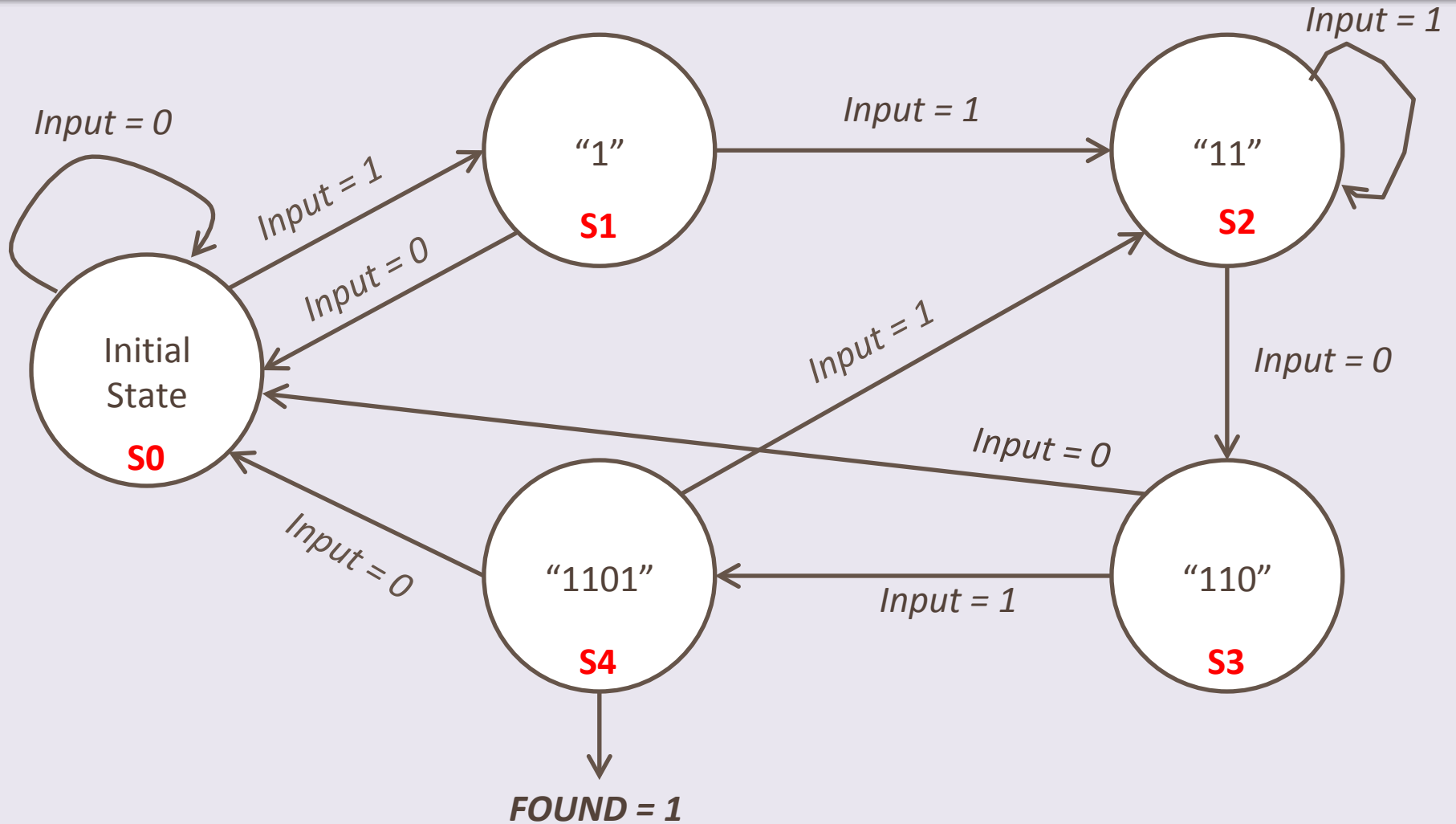

Representing The States

- How many bits do I need to represent all the states in this “Detect 1101” Machine?
- There are 5 unique states (including “init”)
 - So, 3 bits
- How many D-FFs should I have to build this machine?
 - 3 bits = 3 D-FFs

State	S2	S1	S0
Initial	0	0	0
Found “1”	0	0	1
Found “11”	0	1	0
Found “110”	0	1	1
Found “1101”	1	0	0



Designing the Circuit for the FSM

1. We start with a T.T
2. Make K-Maps and simplify
3. Design the circuit



1. The Truth Table




State	S2	S1	S0	I	S2*	S1*	S0*	FOUND
Initial	0	0	0	0	0	0	0	0
				1	0	0	1	0
Found "1"	0	0	1	0	0	0	0	0
				1	0	1	0	0
Found "11"	0	1	0	0	1	1	0	0
				1	0	1	0	0
Found "110"	0	1	1	0	0	0	0	0
				1	1	0	0	0
Found "1101"	1	0	0	0	0	0	0	1
				1	0	1	0	1

2. K-Maps

- Example: for $S2^*$
 - You need to do this for all 4 outputs

$$\begin{aligned} S2^* &= \neg S2.S1.\neg S0.\neg I \\ &+ \neg S2.S1.S0.I \\ &= \neg S2.S1.(\neg S0.\neg I + S0.I) \\ &= \neg S2.S1.\neg(S0 \oplus I) \end{aligned}$$



$S2.S1$	00	01	11	10
$S0.I$				
00		1		
01				
11		1		
10				

3. Design the Circuit

- See blackboard...

The “One Hot” Method

- Most popularly used in building FSMs
- Give each state it's own D-FF output
 - **# of FFs needed = # of states**
 - You end up using MORE D-FFs, but the implementation is easier to automate
- Inputs to the FFs are combinatorial logic that can be simplified into a “sum-of-products” type of Boolean expression
- Current CAD software can do this automatically
- Implementation is usually done on a simulator (software), or prototype hardware Integrated Circuit (FPGA)

Encoding our States

Per the last example: We had 5 separate states:

<u>NAME</u>	<u>Binary Code</u>	<u>"One Hot" Code</u>	<u>OUTPUTS</u>
• Initial State	S0	000	00001
• "1"	S1	001	00010
• "11"	S2	010	00100
• "110"	S3	011	01000
• "1101"	S4	100	10000

FOUND

- Advantage of this "One Hot" approach?
 - When we implement the machine with circuits, we can use a D-FF for every state (so, in this example, we'd use 5 of them)

Using the “One Hot” Code to Determine the Circuit Design

- Every state has 1 D-FF
- We can see that (follow the arrows!!):


$$S1^* = S0.I$$

$$S2^* = S1.I + S2.I + S4.I$$

$$S3^* = S2.\bar{I}$$

$$S4^* = S3.I$$

 
$$S0^* = S0.\bar{I} + S1.\bar{I} + S3.\bar{I} + S4.\bar{I}$$



Also, when S4 happens, FOUND = 1, i.e. **FOUND = S4**

We have now described ALL the outputs of the machine as combinations of certain inputs

Implementing the Circuit

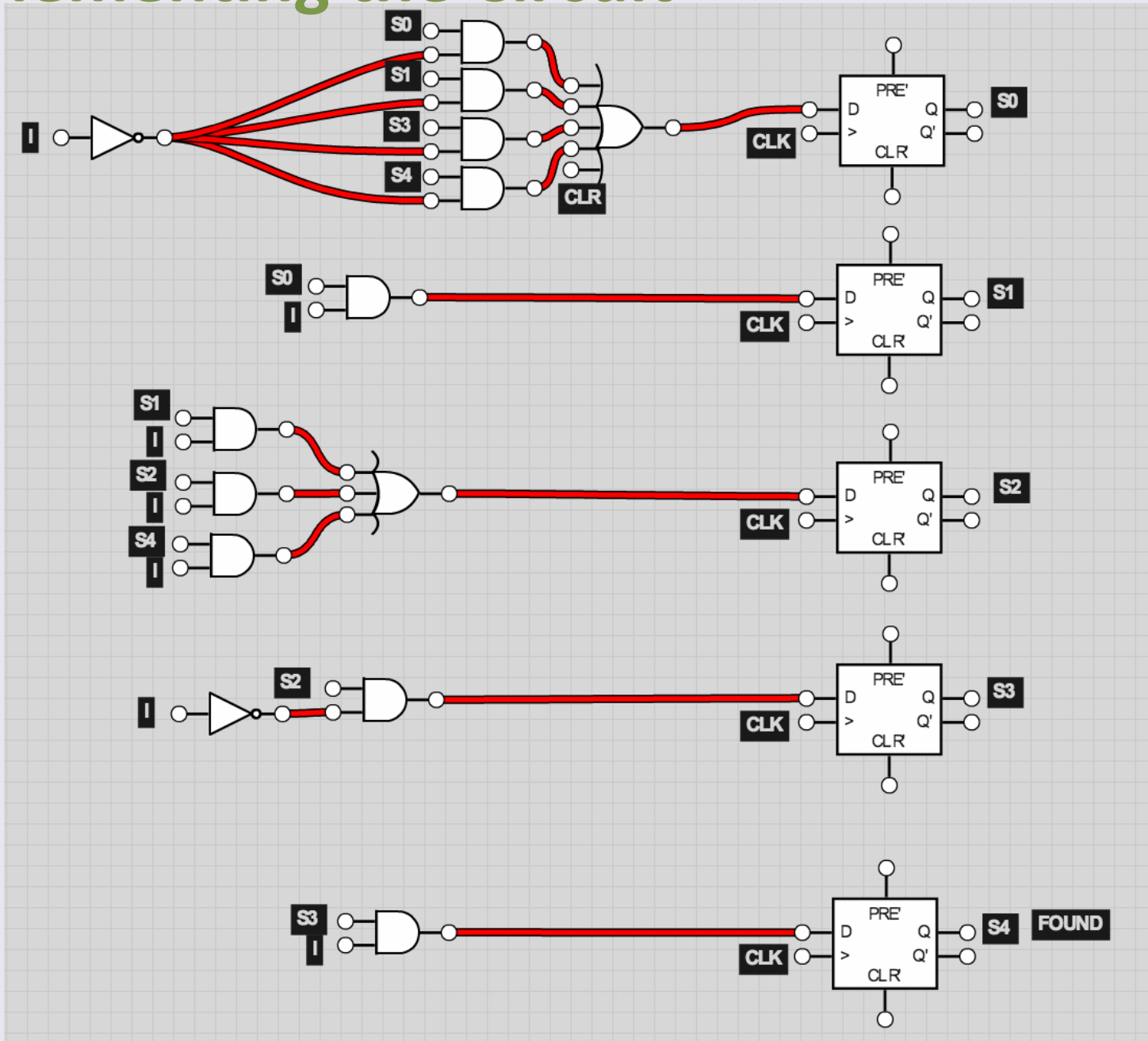

Your To Dos

- Lab #8 is due Monday!
- Lab #9 is on FSM and will be issued tomorrow
 - Due on the last day of classes

</LECTURE>